

Lecture 30: Types of feedback

Feedback in amplifiers

DI02011011: Electronics Circuit and Application (ECA)

Lecture Agenda & Outline

- 1. Mathematical Proofs: Derivation of Input Impedance for Series (KVL) and Shunt (KCL) Mixing
- 2. Mathematical Proofs: Derivation of Output Impedance for Voltage and Current Sampling using Test Sources
- 3. High-Frequency Pole Movement: Root-Locus and Q-factor Dynamics in Multi-Pole Feedback Amplifiers
- 4. Stability Metrics: Gain Margin (GM) and Phase Margin (PM) Criteria on Nyquist and Bode Plots
- 5. Frequency Compensation: Dominant Pole Placement, Lag Compensation, and Miller Pole-Splitting Mechanics
- 6. Engineering Design Examples: Multi-Stage Feedback Calculations and Miller Compensation Design

Mathematical Proof of Input Impedance Transformation

- Proof 1: Series Input Mixing (Voltage Comparison):
- Input Circuit Equations: Apply Kirchhoff's Voltage Law at input loop: $V_s = V_i + V_f$.
Substitute $V_f = \beta V_o = \beta (A * V_i)$.
- Substituting V_f : $V_s = V_i + \beta A V_i = V_i (1 + \beta A)$.
- Input Current Equation: $I_i = V_i / R_{in}$ (where R_{in} is open-loop input resistance).
- Closed-Loop Resistance Derivation: $R_{inf} = V_s / I_i = [V_i (1 + \beta A)] / (V_i / R_{in}) = R_{in} (1 + \beta A)$. PROVED!
- Proof 2: Shunt Input Mixing (Current Comparison):
- Apply Kirchhoff's Current Law at input node: $I_s = I_i + I_f$. Substitute $I_f = \beta I_o = \beta (A * I_i)$.
- Substituting I_f : $I_s = I_i + \beta A I_i = I_i (1 + \beta A)$.
- Input Voltage Equation: $V_i = I_i * R_{in}$.
- Closed-Loop Resistance Derivation: $R_{inf} = V_i / I_s = (I_i R_{in}) / [I_i (1 + \beta A)] = R_{in} / (1 + \beta A)$. PROVED!

Mathematical Proof of Output Impedance Transformation

- Proof Method: Deactivate input signal source (set $V_s = 0$ or $I_s = 0$), apply an external test voltage V_x at output terminals, measure resulting current I_x . $R_{of} = V_x / I_x$.
- Proof 1: Voltage Output Sampling (Shunt Output):
 - For set $V_s = 0$ and applied V_x : Feedback voltage $V_f = \beta V_x$. *Series input gives error* $V_i = 0 - V_f = -\beta V_x$.
 - Internal Amplifier Current: Dependent source generates current $g_m V_i = -A V_x / R_o$.
 - KCL at Output Node: $I_x = (V_x / R_o) - (\text{internal source current}) = (V_x / R_o) - (-A \beta V_x / R_o) = (V_x / R_o) (1 + A \beta)$.
 - Closed-Loop Output Resistance: $R_{of} = V_x / I_x = R_o / (1 + A \beta)$. PROVED!
- Proof 2: Current Output Sampling (Series Output):
 - Applying test current I_x through output loop with $V_s = 0$ gives $V_f = \beta V_x$ $I_x = I$ $V_i = -\beta V_x$.
 - KVL around Output Loop: $V_x = I_x R_o - A V_i = I_x R_o - A (-\beta I_x) = I_x R_o (1 + A \beta)$.
 - Closed-Loop Output Resistance: $R_{of} = V_x / I_x = R_o (1 + A \beta)$. PROVED!

Summary & Matrix of Impedance Transformation Rules

- Master Impedance Matrix:
- Topology 1 (Voltage-Series): Series Input $-i$ $R_{in} = R_{in} (1 + A_v \beta_v)$; Voltage Output $-i$ $R_{of} = R_o / (1 + A_v \beta_v)$.
- Topology 2 (Current-Series): Series Input $-i$ $R_{in} = R_{in} (1 + A_m \beta_z)$; Current Output $-i$ $R_{of} = R_o (1 + A_m \beta_z)$.
- Topology 3 (Voltage-Shunt): Shunt Input $-i$ $R_{in} = R_{in} / (1 + A_r \beta_g)$; Voltage Output $-i$ $R_{of} = R_o / (1 + A_r \beta_g)$.
- Topology 4 (Current-Shunt): Shunt Input $-i$ $R_{in} = R_{in} / (1 + A_i \beta_i)$; Current Output $-i$ $R_{of} = R_o (1 + A_i \beta_i)$.
- Signal Conditioning Matching:
- Voltage Source $-i$ Requires Voltage-Series or Current-Series (High R_{in}).
- Current Source $-i$ Requires Voltage-Shunt or Current-Shunt (Low R_{in}).
- Voltage Load $-i$ Requires Voltage-Series or Voltage-Shunt (Low R_{out}).
- Current Load $-i$ Requires Current-Series or Current-Shunt (High R_{out}).

Frequency Response Dynamics & Pole Movement under Feedback

- Single-Pole System Root Locus: Open-loop transfer function $A(s) = A_0 / (1 + s / \omega_p)$.
- Closed-Loop Transfer Function: $A_f(s) = [A_0 / (1 + s / \omega_p)] / [1 + \beta A_0 / (1 + s / \omega_p)] = [A_0 / (1 + A_0 \beta)] / [1 + s / (\omega_p (1 + A_0 \beta))]$.
- Pole Trajectory: The real pole moves along the negative real axis from $s = -\omega_p$ to $s = -\omega_{pf} = -\omega_p (1 + A_0 \beta)$. System remains UNCONDITIONALLY STABLE for any amount of feedback!
- Two-Pole System Dynamics: Open-loop transfer function $A(s) = A_0 / [(1 + s / \omega_{p1}) * (1 + s / \omega_{p2})]$.
- Complex Conjugate Pole Pair: As feedback factor β increases, the two real poles move toward each other, collide on the real axis, and break out into complex conjugate poles: $s_{1,2} = -\sigma \pm j * \omega_d$.
- Peaking & Over-Shoot: Complex poles induce high-frequency gain peaking in frequency response and transient ringing in step response if quality factor $Q = \sqrt{1 + A_0 * \beta} / (1 + \omega_{p1} / \omega_{p2}) \geq 0.707$.

Multi-Pole Instability & High-Frequency Phase Shift Mechanics

- Three-Pole System Instability: Open-loop transfer function $A(s) = A_0 / [(1 + s / \omega_{p1}) (1 + s / \omega_{p2}) (1 + s / \omega_{p3})]$.
- Phase Accumulation: Each pole contributes up to -90 degrees of phase shift at high frequencies. A 3-pole system accumulates up to -270 degrees of phase lag.
- Phase Crossover Frequency (ω_{180}): Frequency where total phase shift reaches -180 degrees: $\angle(A(j \omega_{180}) \beta) = -180 \text{ deg}$.
- Positive Feedback Transformation: At ω_{180} , $e^{-j 180 \text{ deg}} = -1$. The denominator $(1 + A \beta)$ becomes $(1 - A * \beta)$. Negative feedback transforms into POSITIVE FEEDBACK!
- Barkhausen Runaway Condition: If loop gain magnitude $|A(j \omega_{180}) \beta| \geq 1$ (0 dB), the system undergoes self-sustained spontaneous oscillation.

Gain Margin (GM) and Phase Margin (PM) Stability Criteria

- Bode Plot Stability Evaluation: Plot $20 \log_{10}(|A \beta|)$ and phase angle($A \beta$) versus logarithmic frequency.
- Gain Crossover Frequency (f_c): Defined where $|A(j 2 \pi f_c) \beta| = 1$ (0 dB).
- Phase Crossover Frequency (f_{180}): Defined where $\angle(A(j 2 \pi f_{180}) \beta) = -180^\circ$.
- Phase Margin Formula: $PM = 180^\circ + \angle(A(j 2 \pi f_c) \beta)$.
- PM Target Values: $PM \geq 0^\circ$ for stability; $PM \geq 45^\circ$ for acceptable transient response; $PM = 60^\circ$ for maximally flat Butterworth response (zero peaking).
- Gain Margin Formula: $GM = -20 \log_{10}(|A(j 2 \pi f_{180}) \beta|)$. Target: $GM \geq 6 \text{ dB} - 10 \text{ dB}$.

Frequency Compensation: Dominant Pole & Miller Pole Splitting

- Need for Frequency Compensation: High-gain multistage op-amps have multiple poles, leading to PM $\downarrow$ 0 (unstable). Frequency compensation alters loop response to force $|A \cdot \beta| \gg 1$ before phase reaches -180 degrees.
- Dominant Pole Compensation: Adding a large capacitor C_D across an internal high-resistance node pulls the first pole down to a very low frequency $f_{p1'} \ll f_{p1}$.
- Drawback of Simple Dominant Pole: Drastically reduces open-loop bandwidth and limits amplifier Slew Rate ($SR = dV/dt$).
- Miller Compensation (Pole Splitting): Connecting a small compensation capacitor C_C across the high-gain inverting stage (Stage 2).
- Miller Pole-Splitting Action:
 - 1. Dominant pole f_{p1} is pulled LOW to $f_{p1'}$ approx $1 / [2 \pi (g_{m2} R_1 R_2 * C_C)]$ via Miller input capacitance multiplication.
 - 2. Non-dominant pole f_{p2} is pushed HIGH to $f_{p2'}$ approx $g_{m2} / [2 \pi (C_1 + C_2)]$ via negative feedback around Stage 2!
- Result: Widely separates poles, ensuring 20 dB/decade roll-off through gain crossover frequency and achieving PM approx 60 - 90 degrees!

Effect of Feedback on Noise & Internal Interference

- Noise Source Classification: Input-referred noise V_{ni} (from sensors/first stage) vs Internal stage noise V_{n2} (from power supply ripple, second stage drivers).
- Signal-to-Noise Ratio (SNR) Equation: Output signal $V_o = A_1 A_2 V_s$; Output noise from stage 2 $V_{on} = A_2 * V_{n2}$.
- Closed-Loop SNR Transformation: With feedback factor β applied around overall system:
- $V_{of} = (A_1 A_2 V_s) / (1 + A_1 A_2 \beta)$, and $V_{onf} = (A_2 V_{n2}) / (1 + A_1 A_2 \beta)$.
- System SNR with Feedback: $SNR_f = V_{of} / V_{onf} = (A_1 A_2 V_s) / (A_2 V_{n2}) = A_1 (V_s / V_{n2})$.
- Noise Suppression Conclusion: Negative feedback dramatically suppresses internal noise V_{n2} injected AFTER high-gain stage A_1 . However, noise V_{ni} present at the primary input is amplified along with the signal!

Design Example 1: Multi-Stage Feedback Impedance Analysis

- Problem Statement: A two-stage BJT Series-Shunt (Voltage-Series) feedback amplifier has open-loop voltage gain $A_v = 2,000$ (66 dB), open-loop input resistance $R_{in} = 4 \text{ k-}\Omega$, open-loop output resistance $R_o = 8 \text{ k-}\Omega$. The feedback factor is $\beta_v = 0.025$.
- Step 1: Calculate Loop Gain T : $T = A_v \beta_v = 2,000 \cdot 0.025 = 50$ (33.98 dB).
- Step 2: Calculate Amount of Feedback F : $F = 1 + T = 1 + 50 = 51$ (34.15 dB).
- Step 3: Calculate Closed-Loop Gain A_{vf} : $A_{vf} = A_v / (1 + T) = 2,000 / 51 = 39.215$ (31.87 dB). (Note: Asymptotic $1 / \beta_v = 1 / 0.025 = 40$!).
- Step 4: Calculate Closed-Loop Input Resistance R_{inf} : Series input mixing boosts input resistance: $R_{inf} = R_{in} (1 + T) = 4 \text{ k-}\Omega \cdot 51 = 204 \text{ k-}\Omega$!
- Step 5: Calculate Closed-Loop Output Resistance R_{of} : Voltage output sampling lowers output resistance: $R_{of} = R_o / (1 + T) = 8,000 \text{ }\Omega / 51 = 156.86 \text{ }\Omega$!
- Conclusion: Feedback boosted input resistance from 4 k- Ω to 204 k- Ω , and dropped output resistance from 8 k- Ω to 156.86 Ω .

Design Example 2: Miller Compensation & Phase Margin Calculation

- Problem Statement: An uncompensated op-amp has open-loop gain $A_0 = 10^5$, primary pole $f_{p1} = 100$ Hz, secondary pole $f_{p2} = 1$ MHz, and tertiary pole $f_{p3} = 10$ MHz. Calculate Phase Margin with $\beta = 0.1$, and design Miller capacitor C_C for $PM = 60$ deg.
- Step 1: Uncompensated Phase Margin at Gain Crossover: Loop gain $T(0) = 10^5 \cdot 0.1 = 10^4$ (80 dB). Uncompensated crossover frequency f_c approx 100 Hz $10^4 = 1$ MHz.
- At $f_c = 1$ MHz: Phase lag $\angle(T) = -\arctan(1M / 100) - \arctan(1M / 1M) - \arctan(1M / 10M) = -90 \text{ deg} - 45 \text{ deg} - 5.7 \text{ deg} = -140.7 \text{ deg}$.
- Uncompensated Phase Margin: $PM = 180 \text{ deg} - 140.7 \text{ deg} = 39.3 \text{ deg}$ (Inadequate! Target $PM = 60 \text{ deg}$).
- Step 2: Miller Pole-Splitting Design for $PM = 60$ deg: For $PM = 60 \text{ deg}$, new gain crossover $f_{c'}$ must equal non-dominant pole $f_{p2'} = 1$ MHz.
- Required New Dominant Pole $f_{p1'}$: $f_{c'} = f_{p1'} \quad T(0) = 1 \text{ MHz} = f_{p1'} \cdot 10^4 \Rightarrow f_{p1'} = 100 \text{ Hz} / 10 = 10 \text{ Hz}$.
- Step 3: Calculating Miller Capacitor C_C : Given stage 1 output resistance $R_1 = 1 \text{ M-Ohm}$ and stage 2 transconductance $g_{m2} = 5 \text{ mS}$:
- $f_{p1'} = 1 / [2 \pi g_{m2} R_1 R_2 C_C] \Rightarrow C_C = 1 / [2 \pi \cdot 5 \text{ mS} \cdot 1 \text{ M-Ohm} \cdot 10 \text{ k-Ohm} \cdot 10 \text{ Hz}] = 3.18 \text{ pF}$.

Multi-Variable Design Trade-offs: Gain vs Bandwidth vs Stability

- 1. Voltage Gain vs Bandwidth Trade-Off: Increasing feedback factor β lowers closed-loop voltage gain A_f , but expands system bandwidth $f_{Hf} = f_H (1 + A_0 \beta)$ proportionally.
- 2. Gain Margin / Phase Margin vs Loop Gain Trade-Off: High loop gain $T = A * \beta$ provides superior gain desensitization and distortion reduction, but pushes multi-pole systems toward phase crossover, degrading Phase Margin.
- 3. Input/Output Impedance Matching: Series input boosts R_{in} (ideal for voltage sensing); Shunt input lowers R_{in} (ideal for current sensing). Voltage sampling lowers R_{out} ; Current sampling boosts R_{out} .
- 4. Power & Area Overhead: Miller compensation requires silicon area for capacitor C_C and increases high-frequency power dissipation during large-signal slewing.
- Engineering Synthesis: Active circuit design demands balancing gain requirements, load impedance matching, noise figure, and Phase Margin $\phi = 60$ degrees.

Unit 4 Comprehensive Summary & Master Takeaways

- Closed-Loop Fundamental Formula: $A_f = A / (1 + A \beta)$. Under heavy feedback ($A \beta \gg 1$), $A_f \approx 1 / \beta$.
- Universal Impedance Modification: All input and output impedances are transformed by factor $(1 + \text{Loop Gain}) = (1 + A * \beta)$.
- Series Input $\rightarrow R_{in} = R_{in} (1 + A \beta)$; Shunt Input $\rightarrow R_{in} = R_{in} / (1 + A * \beta)$.
- Voltage Output $\rightarrow R_{of} = R_o / (1 + A \beta)$; Current Output $\rightarrow R_{of} = R_o (1 + A * \beta)$.
- Stability Criterion: Stable amplifier operation requires Phase Margin $PM \geq 45^\circ$ (60° optimal) and Gain Margin $GM \geq 6 \text{ dB}$.
- Miller Compensation: Uses pole splitting via capacitor C_C to pull primary pole down and push secondary pole up, guaranteeing unconditional stability.